



**A A B University**

**Faculty of Computer Sciences**

---

**Introduction to Digital Technologies and Circuits**

**Week 13:**


## **Registers and Counters**

**Asst. Prof. Dr. Mentor Hamiti**  
[mentor.hamiti@universitetiaab.com](mailto:mentor.hamiti@universitetiaab.com)

---



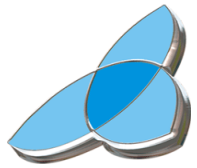- A circuit with flip-flops is considered a sequential circuit even in the absence of combinational logic.
- Circuits that include flip-flops are usually classified by the function they perform. Two such circuits are:
  - **Registers** and
  - **Counters**



## ■ Register

- is a group of flip-flops. Its basic function is to hold information within a digital system so as to make it available to the logic units during the computing process. However, a register may also have additional capabilities associated with it.



## ■ Counter

- is essentially a register that goes through a predetermined sequence of states. The gates in the counter are connected in such a way as to produce the prescribed sequence of binary states.




- Counters are frequently used in computers and other digital systems:
  - Event Counting,
  - Frequency Division,
  - Timing and Control Operations
  
- Like all other sequential logic circuits, counter circuits can be classified into two categories: **asynchronous** and **synchronous**.
  - In synchronous counters all memory elements are simultaneously triggered by a clock, whereas in asynchronous counters the output of each memory element activates the next memory element.
  
- Many types of counters are used in practice:
  - In some cases they count in pure binary; in other cases the count may differ considerably from straight binary (e.g., decade, BCD counters,  $\text{MOD} < 2^N$  counters, est.).

# Asynchronous Counters

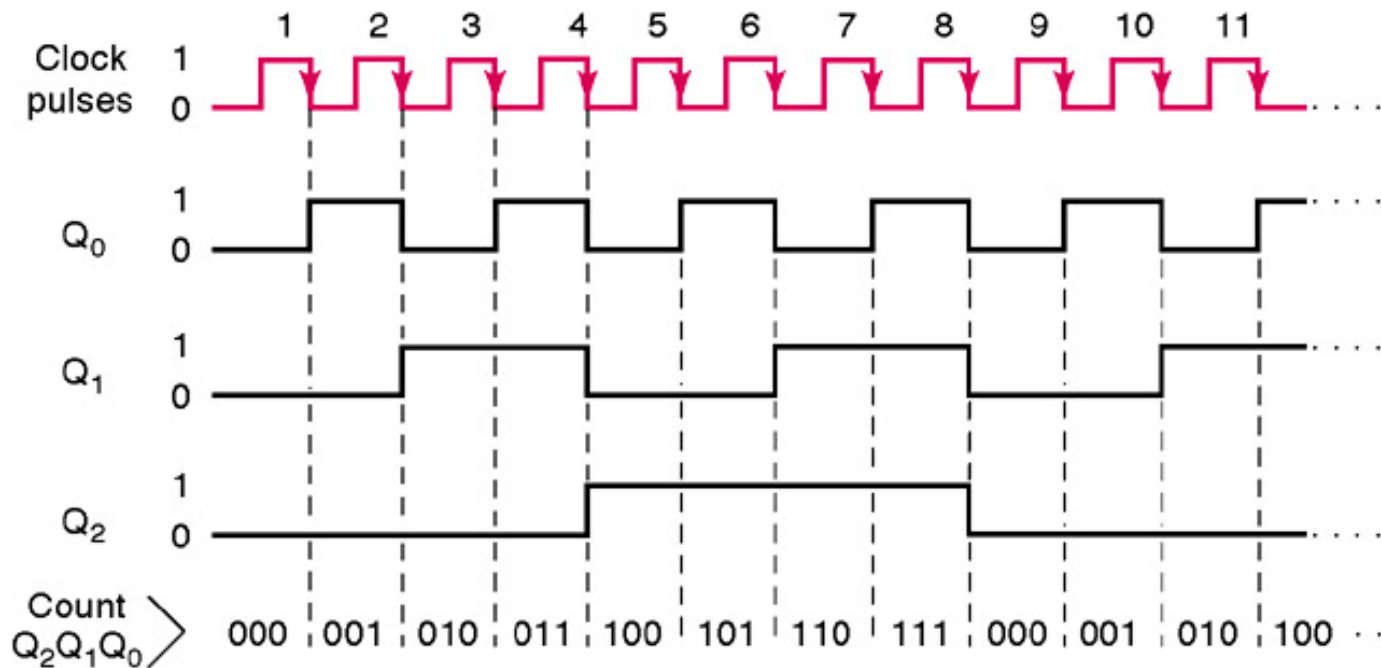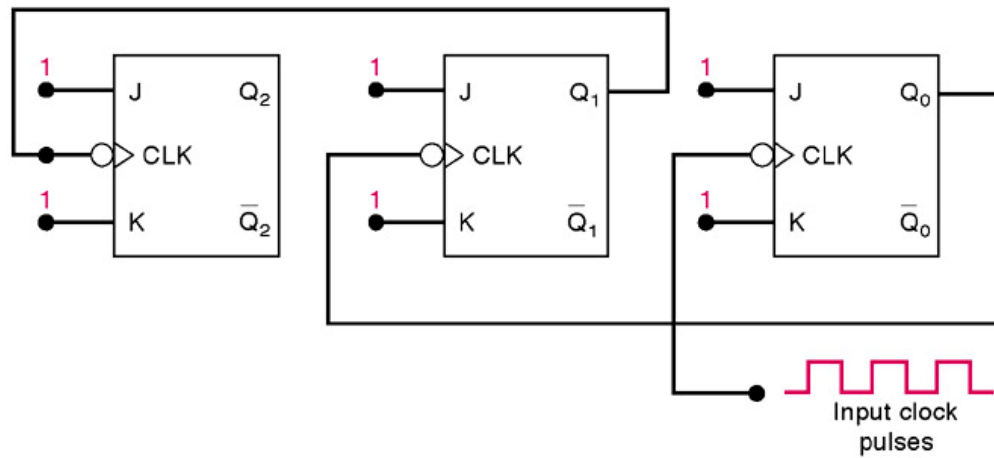



- Example 1:

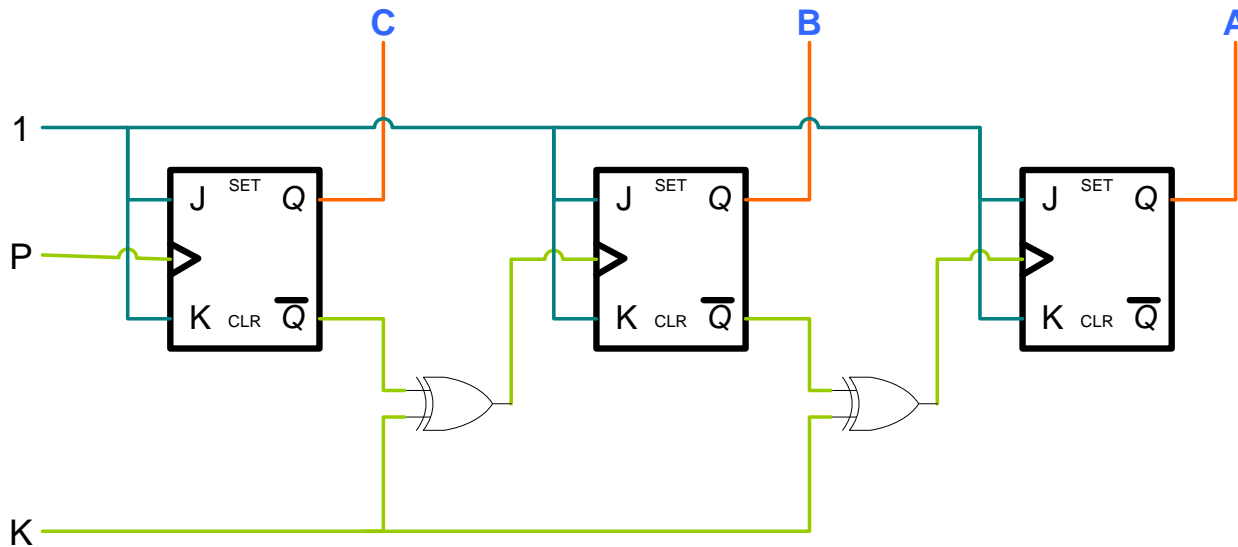

- Timing Diagrams...

# Synchronous Counters


---



- A synchronous counter connects all of its flip-flop clock inputs to the same common CLK signal, so that all of the flip-flop outputs change at the same time!
  - after only  $t_F$  ns of delay ( $t_F$  is the propagation delay from input to output of the flip-flop)




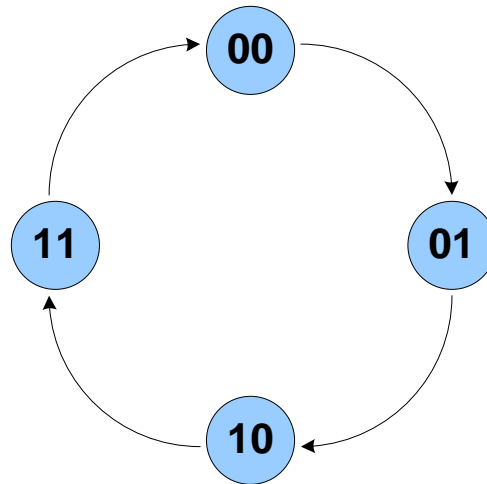- Example 2:
  - Design a synchronous BCD counter described with the following state diagram:



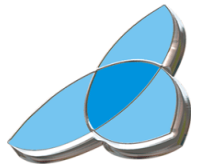- Using:
  - a) JK - Flip-Flops
  - b) T - Flip-Flops
  - c) D - Flip-Flops






- Example 3:
  - Design the counter with the following predetermined sequence of states:

**001   011   101   111**


- Increment other states to the next one!
- Use Flip-Flops:
  - a) JK - Flip-Flops
  - b) T - Flip-Flops
  - c) D - Flip-Flops

and basic logic gates:

# Counters with $MOD < 2^N$

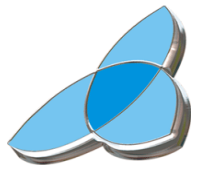

- MOD 6 <  $2^N$

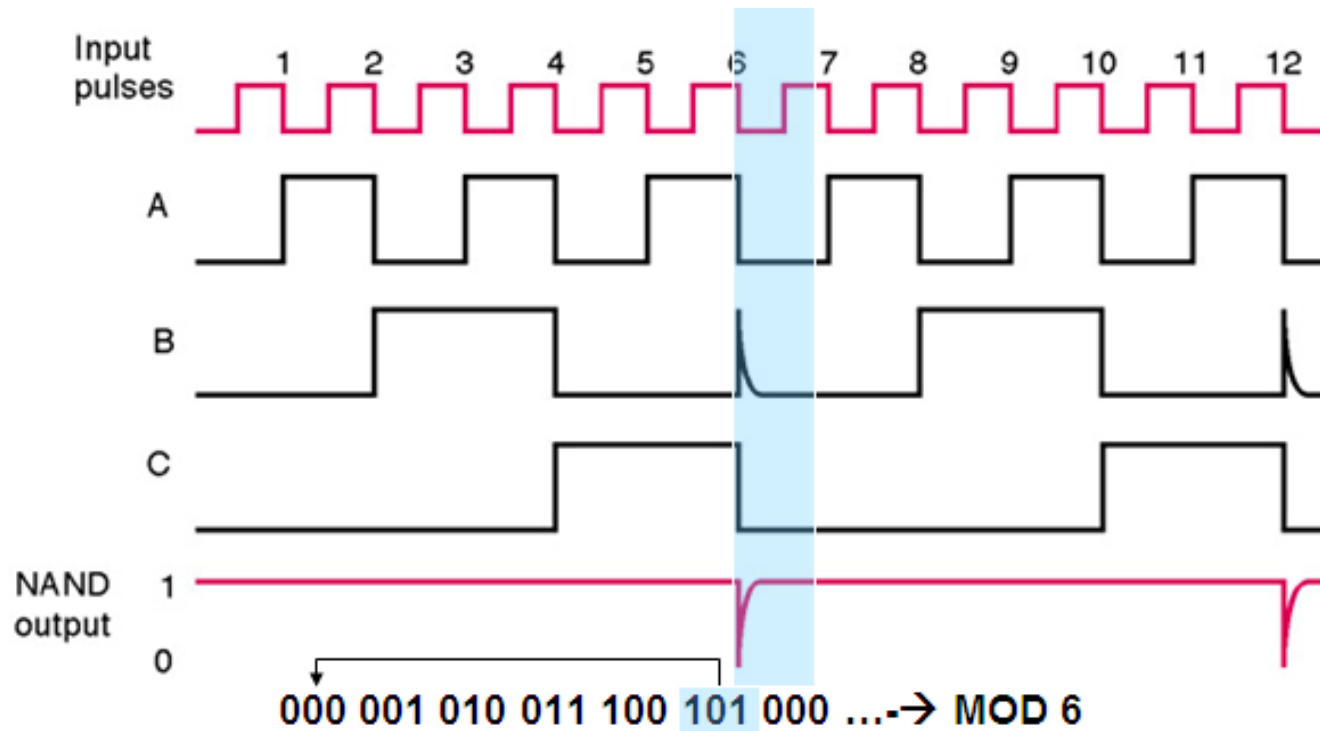



- Questions?!

