



**A A B University**

**Faculty of Computer Sciences**

---

**Introduction to Digital Technologies and Circuits**

**Week 11:**


## **Sequential Logic Circuits**

**Asst. Prof. Dr. Mentor Hamiti**  
[mentor.hamiti@universitetiaab.com](mailto:mentor.hamiti@universitetiaab.com)

---



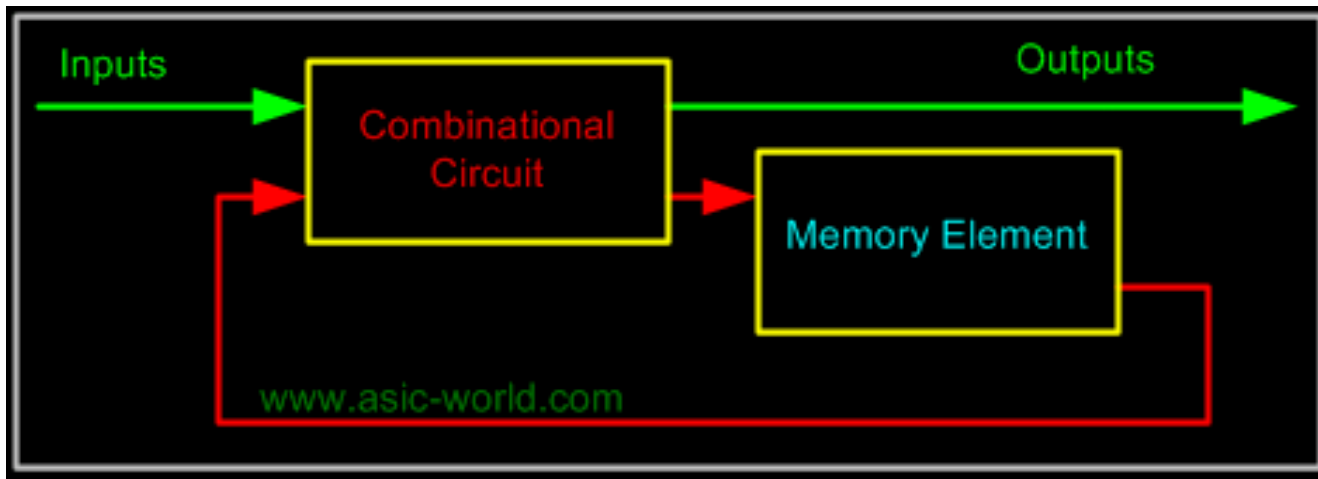
- There are two types of Digital Logic Circuits:
  - Combinational Logic Circuits
  - Sequential Logic Circuits




- Combinational logic output depends on the inputs levels, whereas sequential logic output depends on stored levels and also the input levels.



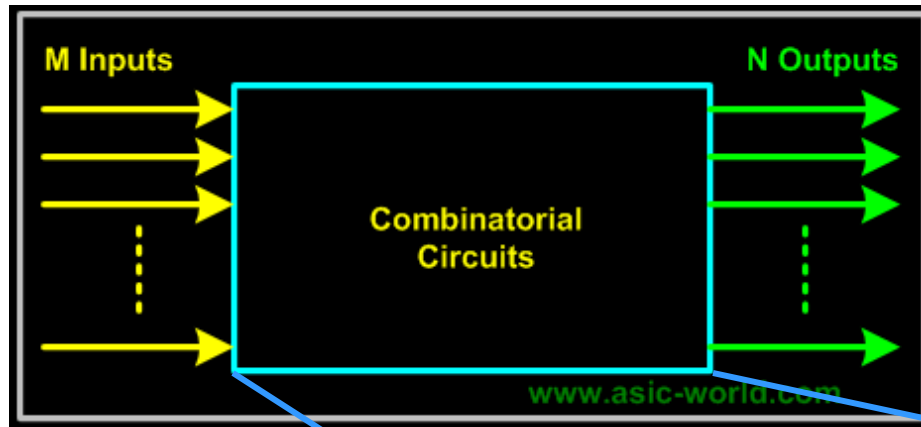- All Combinational Circuits are composed by simple combinational logic elements - “**Logic Gates**”.



 
- Logic Gates:
  - Basic Logic Gates
  - Universal Logic Gates
  - Exclusive Logic Gates


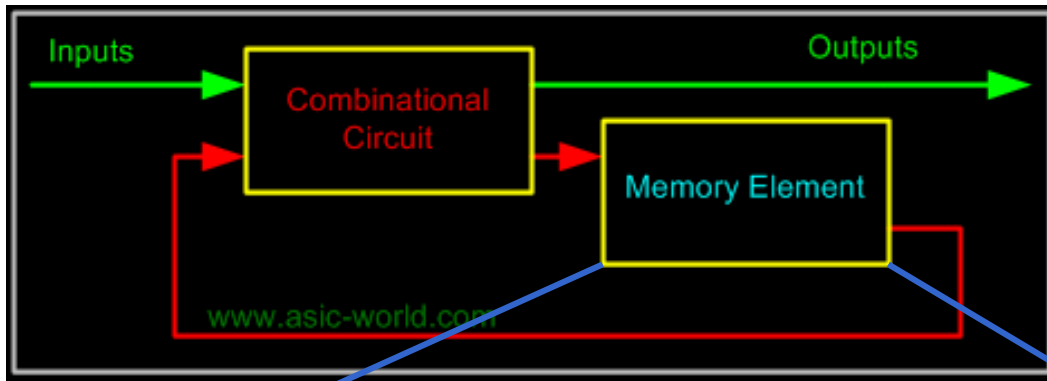
# Sequential Logic Circuits




- **"Flip-flop"** is the common name given to two-state devices which offer basic memory for sequential logic operations.



*Sequential logic differs from combinational logic in that the output of the logic device is dependent not only on the present inputs to the device, but also on past inputs; i.e., the output of a sequential logic device depends on its present internal state and the present inputs. This implies that a sequential logic device has some kind of memory of at least part of its "history" (i.e., its previous inputs).*


- **S-R**
- **J-K**
- **D**
- **T**

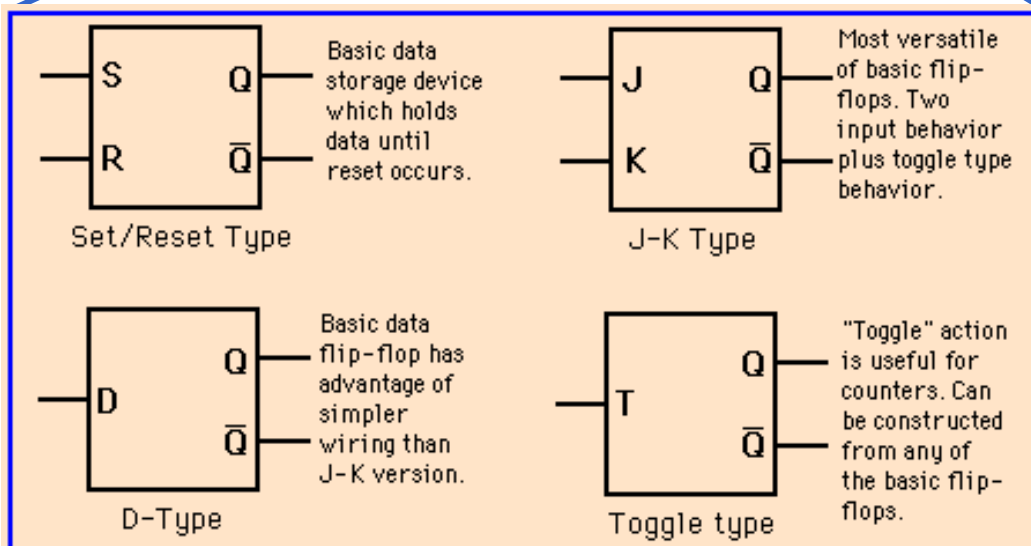


 
## Types of Sequential Logic Circuits:

- A **synchronous** sequential circuit uses a clock to order events
  - a clock is a circuit that emits a series of electrical pulses
  - state changes in sequential circuits only occur when the clock ticks



- **Asynchronous** sequential circuits become active the moment any input value changes

# Flip-Flops (Memory Elements)



---



- Flip-flops can maintain a binary state (i.e. store a bit) indefinitely
- Major differences amongst flip-flops are the number of inputs they possess and the manner in which the inputs affect the current state
- There are four types of flip-flops:
  - **SR**
  - **JK**
  - **D**
  - **T**



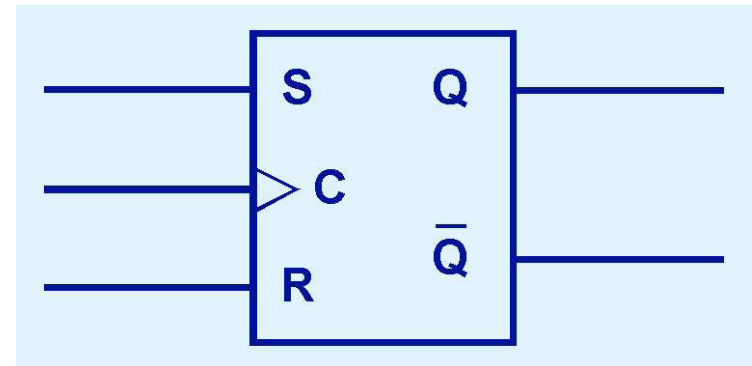
 
- Also known as the Set-Reset Latch (SR-Latch)
  - one of the most basic memory components
  - consists of a pair of interconnected NOR gates that allows the output to be set to 1 and reset to 0


  
# SR flip-flop




- Operation when  $S = 0$ , and  $R = 0$ 
  - if  $Q = 1$  then it remains so, while  $Q' = 0$
  - if  $Q = 0$  then it remains so, while  $Q' = 1$







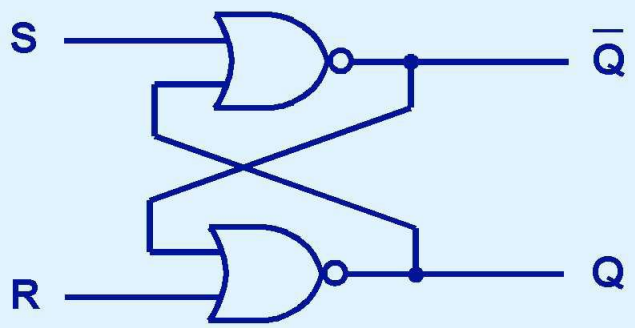- The behavior of an SR-Latch can be described by a **characteristic table**
  - $Q(t)$  means the value of the output at time  $t$
  - $Q(t+1)$  is the value of the output after the next clock pulse



S	R	$Q(t+1)$
0	0	$Q(t)$ (no change)
0	1	0 (reset to 0)
1	0	1 (set to 1)
1	1	undefined




- The SR-latch has three inputs S, R and its current output, Q
- A **truth table** can be constructed for this circuit
- There are two undefined values:
  - when  $S = 1$ , and  $R = 1$  the SR-Latch is undefined (because Q and Q' both equal 0)

Present State		Next State	
S	R	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	undefined
1	1	1	undefined

# SR flip-flop



- State Diagram:

 


Present State		Next State
S	R	Q(t+1)
0	0	0
0	0	1
0	1	0
0	1	0
1	0	1
1	0	1
1	1	undefined
1	1	undefined
 
# Clocked SR flip-flop





- The inputs S and R are enabled by a clock pulse (**CP**)
  - E.g. when the clock pulse is low, no state changes occur


  
# JK flip-flop



- The SR-Latch can be modified to provide a stable state when both inputs S and R are 1
- This modified circuit is called a JK flip-flop






- The characteristic truth table for the JK flip-flop shows the flip-flop is stable for all inputs
  - the J input alone performs the **set** function
  - the K input alone performs the **reset** function
  - if  $J = 1$  and  $K = 1$ , the output is **toggled** or reversed

J	K	$Q(t+1)$
0	0	$Q(t)$ (no change)
0	1	0 (reset to 0)
1	0	1 (set to 1)
1	1	$\bar{Q}(t)$




- State Diagram:

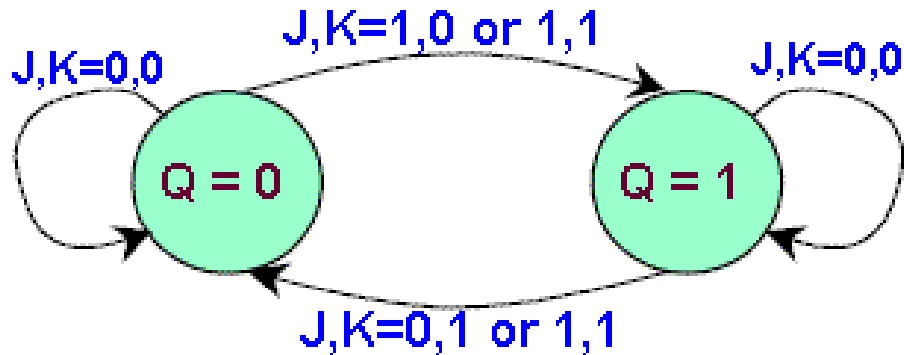


J	K	$Q(t+1)$
0	0	$Q(t)$ (no change)
0	1	0 (reset to 0)
1	0	1 (set to 1)
1	1	$\bar{Q}(t)$



 - The **D** (data) **flip-flop** is another variant of the SR-Latch



 - The output of the circuit only changes when D changes – it remains the same otherwise
  - the circuit stores 1 bit of information and can be used to implement computer memory




D	Q (t+1)
0	0
1	1



# D flip-flop





- State Diagram:

 

D	$Q(t+1)$
0	0
1	1



  - The **T** (toggle) **flip-flop** is another variant of the SR-Latch




- Characteristic Table for T Flip-Flop:

$T(t)$	$Q(t)$	$Q(t + 1)$	Condition
0	0	0	No change
0	1	1	
1	0	1	Toggle
1	1	0	



- State Diagram:

 

$T(t)$	$Q(t)$	$Q(t+1)$	Condition
0	0	0	No change
0	1	1	
1	0	1	Toggle
1	1	0	



- Example 1:
  - Realize the *flip-flop* of type **T** using **D** *flip-flop*!

Starting from:


T	Q	Q <sup>+</sup>	D
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

- Example 2:
  - Realize the *flip-flop* of type **JK** using **T** *flip-flop*!


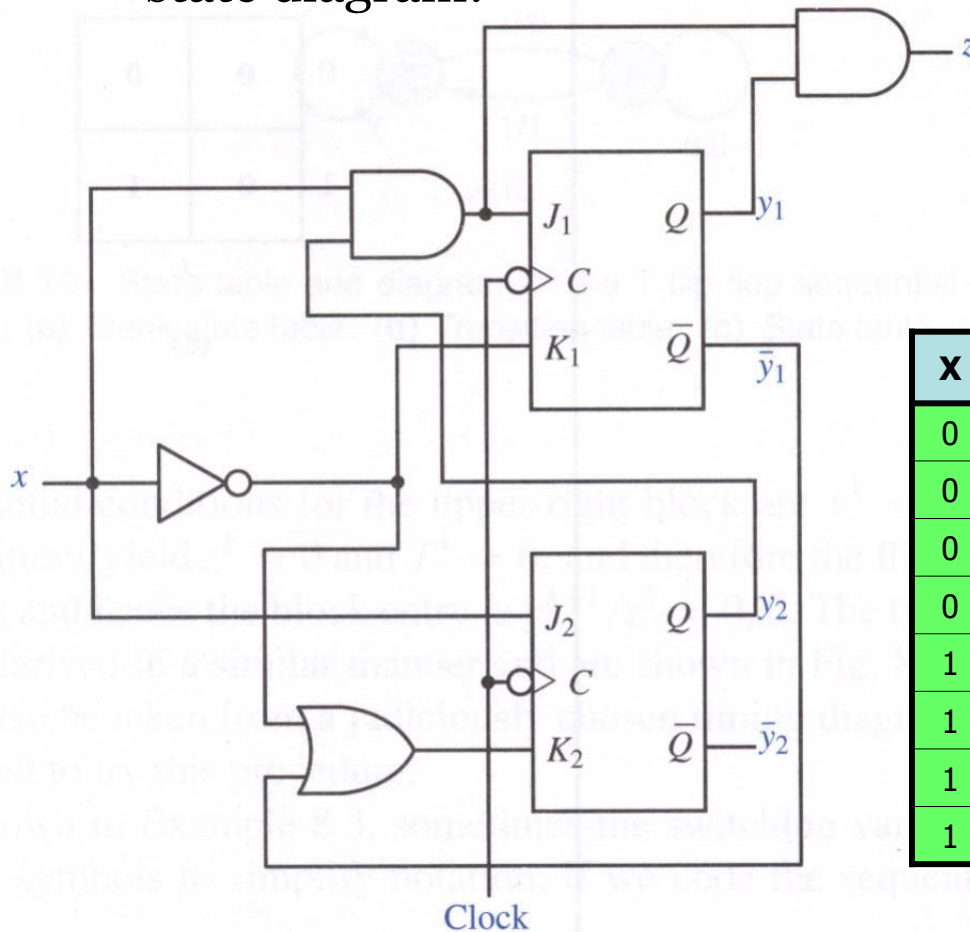
## ■ Example 3:

- For the following sequential logic circuit, find the state table and state diagram!



X	Q <sub>1</sub>	Q <sub>2</sub>	J <sub>1</sub>	K <sub>1</sub>	J <sub>2</sub>	K <sub>2</sub>	Z	Q <sub>1</sub> <sup>+</sup>	Q <sub>2</sub> <sup>+</sup>
0	0	0							
0	0	1							
0	1	0							
0	1	1							
1	0	0							
1	0	1							
1	1	0							
1	1	1							



- Questions?!

