



A A B University

Faculty of Computer Sciences

Introduction to Digital Technologies and Circuits

Week 4:

Boolean Algebra and Logic Functions

Asst. Prof. Dr. **Mentor Hamiti**
mentor.hamiti@universitetiaab.com



- *Binary Arithmetic*
 - *Addition*
 - *Subtraction*
 - *Multiply*
 - *Divide*

- *Octal Arithmetic*

- *Hexadecimal Arithmetic*

- *Binary Codes*
 - *Weighted Codes*
 - *Non Weighted Codes*



- Boolean Algebra
- Logic (Boolean) Functions
- Representations of Boolean Functions
 - Switching Circuits
 - Truth Tables
 - Timing Diagrams
 - Venn Diagrams
 - K-Diagrams



- Let $\mathbf{B}=\{0, 1\}$,

we can define three operations: $+$, \cdot and $'$ on \mathbf{B} as follows:

$+$	1	0
1	1	1
0	1	0

\cdot	1	0
1	1	0
0	0	0

$'$	
1	0
0	1

In other words:

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

$$0 * 0 = 0$$

$$0 * 1 = 0$$

$$1 * 0 = 0$$

$$1 * 1 = 1$$

$$\overline{0} = 1$$

$$\overline{1} = 0$$

- The operations $+$, \cdot and $'$ on $\mathbf{B}=\{0, 1\}$ are called *Boolean sum* (the logical **OR**), *Boolean product* (the logical **AND**) and *Boolean Complementation* (the logical **NOT**)!



- Definition: The set $\mathbf{B}=\{0, 1\}$ together with Boolean $+$, \cdot and $'$ is called a **Boolean Algebra**.
- A **Boolean expression** is a sequence of **zeros**, **ones**, and *literals* separated by **Boolean operators**.
- A **literal** is a primed (negated) or unprimed **variable name**. For our purposes, all variable names will be a single alphabetic character (Ex. A, B, C, X, Y, ...)
- A **Boolean function** is a specific Boolean expression; we will generally give Boolean functions the name “F” with a possible subscript. For example, consider the following Boolean: **$F_0 = AB+C$**

Postulates and Theorems



- For any given algebra system, there are some initial assumptions, or *postulates*, that the system follows. We can deduce additional rules, theorems, and other properties of the system from this basic set of postulates.

- Postulates:

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

$$0 * 0 = 0$$

$$0 * 1 = 0$$

$$1 * 0 = 0$$

$$1 * 1 = 1$$

$$\overline{0} = 1$$

$$\overline{1} = 0$$

- Theorems:

$$A + 0 = A$$

$$A + 1 = 1$$

$$A + A = A$$

$$1 + \overline{A} = 1$$

$$A * 0 = 0$$

$$A * 1 = A$$

$$A * A = A$$

$$A * \overline{A} = 0$$

$$\overline{\overline{A}} = A$$

Postulates and Theorems



- We can prove all other theorems in Boolean algebra using these postulates, but we will not go into the formal proofs of these theorems, however, it is a good idea to familiarize our self with some important theorems in Boolean algebra. A sampling include:

$$(A + B)' = A' \cdot B'$$

or

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

DeMorgan's Theorems

$$(A \cdot B)' = A' + B'$$

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

$$A + A \cdot B = A$$

$$A \cdot (A + B) = A$$

$$A + A'B = A + B$$

$$A' \cdot (A + B') = A'B'$$

$$AB + AB' = A$$

$$(A'+B') \cdot (A' + B) = A'$$

.....

Dual and Inverse Functions



- For every Boolean (**Logic**) **Function**:

$$a) F = A \cdot B + C \quad b) F = A \cdot \bar{B} + \bar{A} \cdot B \quad c) F = A \cdot B + C \cdot (\bar{A} + B)$$

- If in *Logic Function* the result is *Dual Function*:

0 → 1
1 → 0
+ → ·
· → +

$$a) F_d = (A + B) \cdot C \quad b) F_d = (A + \bar{B}) \cdot (\bar{A} + B) \quad c) F_d = (A + B) \cdot [C + (\bar{A} \cdot B)]$$

- If in *Dual Function* the result is *Inverse Function*:

A → \bar{A}
 \bar{A} → A

$$a) \bar{F} = (\bar{A} + \bar{B}) \cdot \bar{C} \quad b) \bar{F} = (\bar{A} + B) \cdot (A + \bar{B}) \quad c) \bar{F} = (\bar{A} + \bar{B}) \cdot [\bar{C} + (A \cdot \bar{B})]$$






- I. Switching Circuits**
- II. Truth Tables**
- III. Timing Diagrams**
- IV. Venn Diagrams**
- V. K-Diagrams**

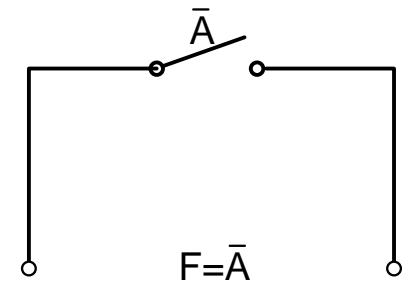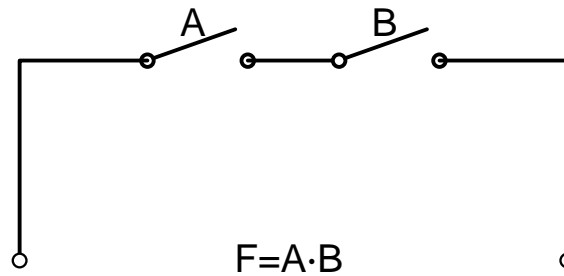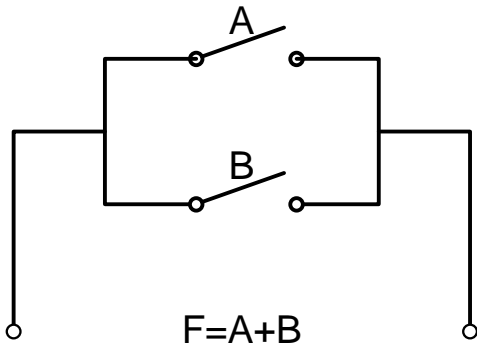I. Switching Circuits



- Representations of Boolean Functions with Switching Circuits:





- Example 1:

- *Draw the circuits for the following functions:*

a) $F_1 = A \cdot B + C$

b) $F_2 = A \cdot \bar{B} + \bar{A} \cdot B$


c) $F_3 = A \cdot B + C \cdot (\bar{A} + B)$

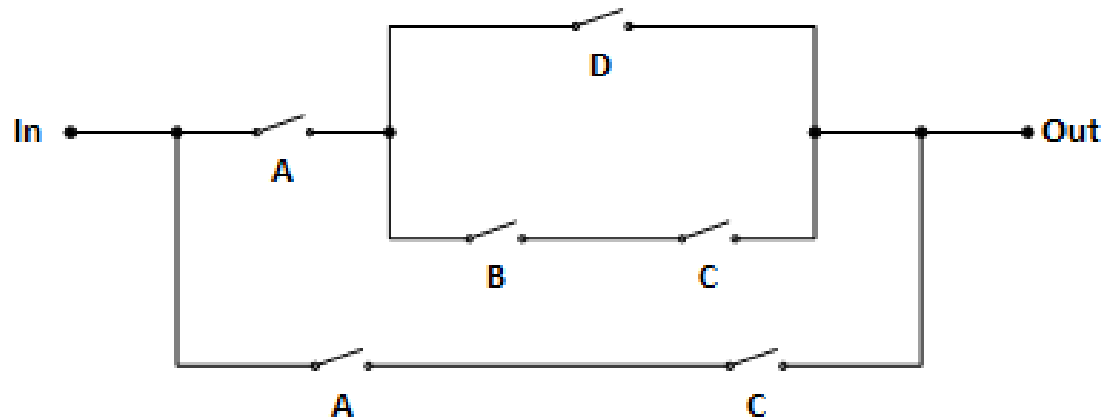I. Switching Circuits



■ Example 2:

- *For the following circuit, find the output and design a simpler circuit that has the same output!*



F = ?

II. Truth (Combinational) Tables



- Representations of Boolean Functions with Combinational Tables:

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

$$F = A + B$$

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

$$F = A \cdot B$$

A	F
0	1
1	0

$$F = \bar{A}$$

II. Truth (Combinational) Tables



- **Minterms and Maxterms**

- The sum of minterms functions form:

$$F = \sum_{i=0}^{2^n - 1} F_i \cdot m_i$$

- The product of Maxterms functions form:

$$F = \prod_{i=0}^{2^n - 1} (F_i + M_i)$$

II. Truth (Combinational) Tables



■ Example 3:

- *Draw the Truth (Combinational) Tables for the following functions:*

$$a) \quad F_1 = A \cdot B + C$$

$$b) \quad F_2 = A \cdot \bar{B} + \bar{A} \cdot B$$

$$c) \quad F_3 = A \cdot B + C \cdot (\bar{A} + B)$$

II. Truth (Combinational) Tables



■ Example 4:

- *For the given Truth Tables, find the logic functions!*

a)

i	A	B	C	F_1
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$F_1(A, B, C) = ?$$

b)




i	F_2
0	0
1	0
2	1
3	1
4	1
5	1
6	0
7	0

$$F_2 = ?$$

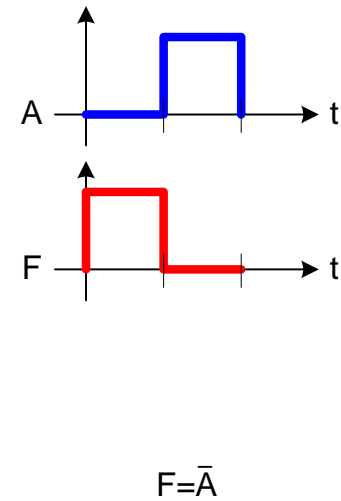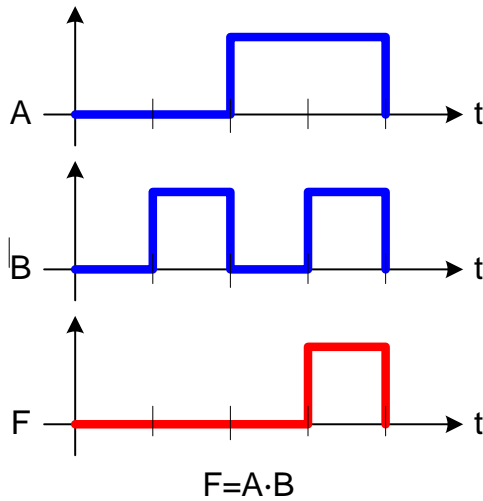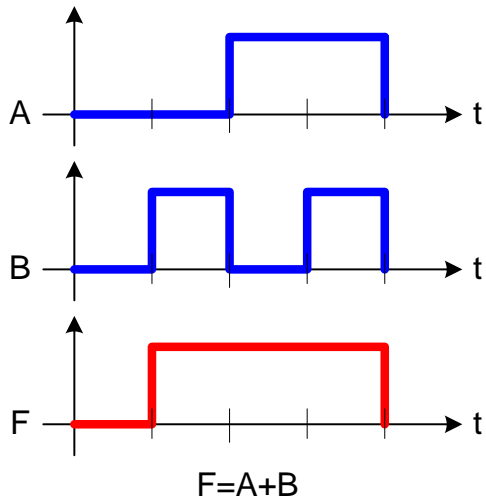III. Timing Diagrams



- Representations of Boolean Functions with Timing Diagrams:



III. Timing Diagrams



- Example 5:

- *Draw the Timing Diagrams for the following functions:*

a) $F_1 = A \cdot B + C$

b) $F_2 = A \cdot \bar{B} + \bar{A} \cdot B$

c) $F_3 = A \cdot B + C \cdot (\bar{A} + B)$

III. Timing Diagrams



■ Example 6:

• *For the given Timing Diagram:*

a) *Find the logic function and*


b) *Simplify the function and draw the minimized circuit*



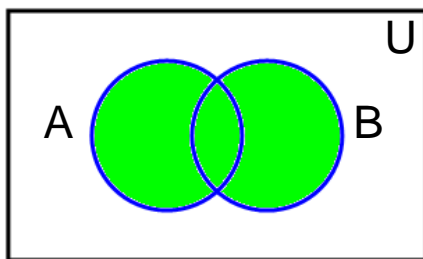
IV. Venn Diagrams




- Representations of Boolean Functions with Venn Diagrams:



$$F=A+B$$

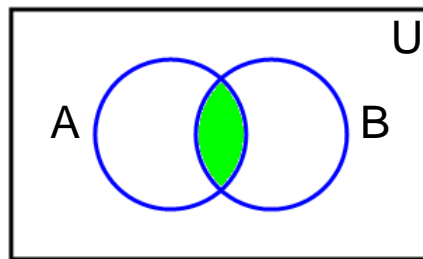

$$F=A \cdot B$$

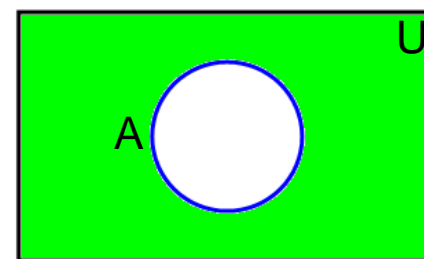

$$F=\bar{A}$$

IV. Venn Diagrams



■ Example 7:

- *Draw the Venn Diagrams for the following functions:*

$$a) \quad F_1 = A \cdot B + C$$

$$b) \quad F_2 = A \cdot \bar{B} + \bar{A} \cdot B$$


$$c) \quad F_3 = A \cdot B + C \cdot (\bar{A} + B)$$

IV. Venn Diagrams



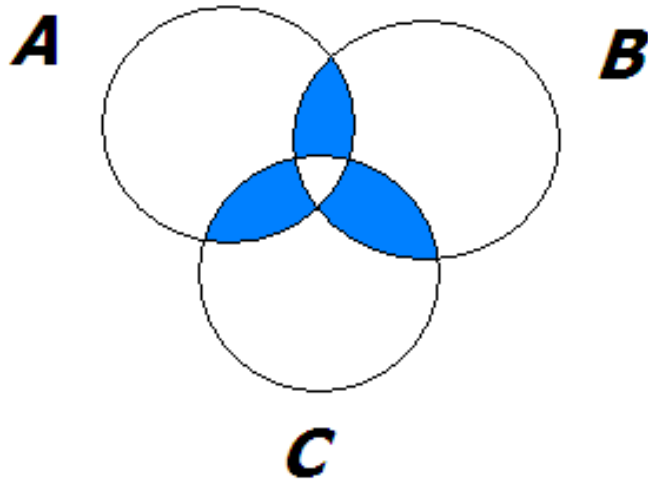- Example 8:

- *For the given Venn Diagram, find the logic function :*




$$F(A, B, C) = ?$$

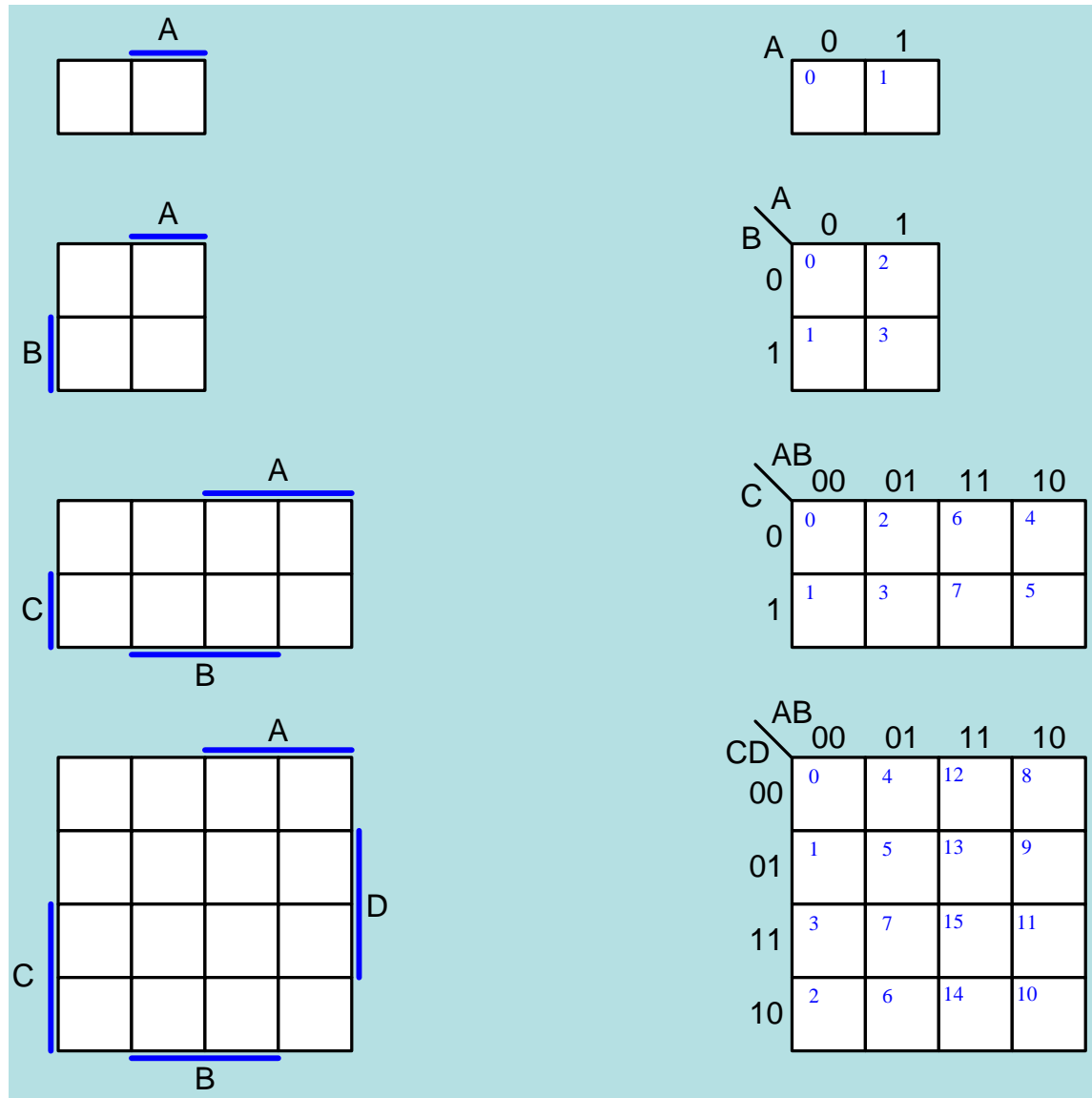V. K-Diagrams



- Representations of Boolean Func. with K-Diagrams (*Karnaugh Diag*):





- Example 9:

- *Draw the K-Diagrams for the following functions:*

a) $F_1 = A \cdot B + C$

b) $F_2 = A \cdot \bar{B} + \bar{A} \cdot B$

c) $F_3 = A \cdot B + C \cdot (\bar{A} + B)$

V. K-Diagrams



■ Example 10:

- For the given K-Diagram, find:

a) The logic function and

b) The Invers function

$$F = ?$$

$$\overline{F} = ?$$

			1	
		1		
1	1			
1	1			

A

B

C

D



- Questions?!

