



A A B University

Faculty of Computer Sciences

Introduction to Digital Technologies and Circuits

Week 8:

Arithmetic Circuits

Asst. Prof. Dr. Mentor Hamiti
mentor.hamiti@universitetiaab.com



- **Combinational Logic Circuits**
 - Decoders
 - Encoders
 - Multiplexers
 - De-multiplexers
 - Other Combinational Circuits



- Combinational Arithmetic Circuits
 - Adders
 - Sub tractors
 - Multipliers
 - Dividers
 - Other Circuits



- Arithmetic circuits are the ones which perform arithmetic operations like: addition, subtraction, multiplication, division, parity calculation, etc.

- Most of the time, designing these circuits is the same or similar as designing:
 - Encoders,
 - Decoders,
 - Multiplexers,
 - De-multiplexers,
 - Code converters, etc.



- Adders are the basic building blocks of all arithmetic circuits
- Adders add two binary numbers and give out sum and carry as output
 - Example: $X + Y = S + c$
- Basically we have two types of adders:
 - Half Adder.
 - Full Adder.



- Adding two single-bit binary values **X**, **Y** produces a sum **S** bit and a carry out **C**-out bit. This operation is called half addition and the circuit to realize it is called a half adder.
- Truth Table:

X	Y	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S(X,Y) = m^1(1,2) = X'Y + XY' = X \oplus Y$$

$$CARRY(X,Y) = m^1(3) = X \cdot Y$$


Half Adder




$$S(X,Y) = m^1(1,2) = X'Y + XY' = X \oplus Y$$

$$CARRY(X,Y) = m^1(3) = X \cdot Y$$

Circuit:

 

Symbol:

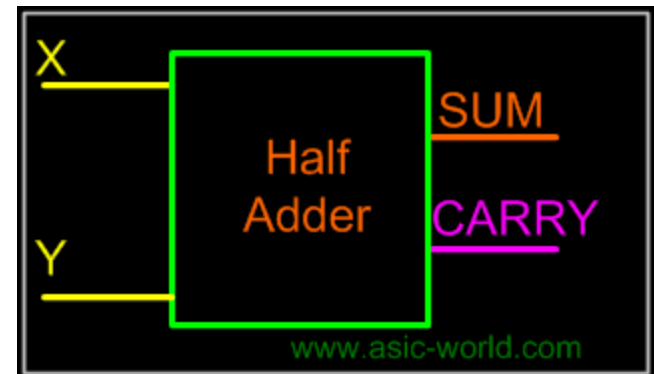

Full Adder




- Full adder takes a three-bit input. Adding two single-bit binary values X, Y with a carry input bit C-in produces a sum bit S and a carry out C-out bit.


- Truth Table:

X	Y	Z	SUM	CARRY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- K-Diagrams:

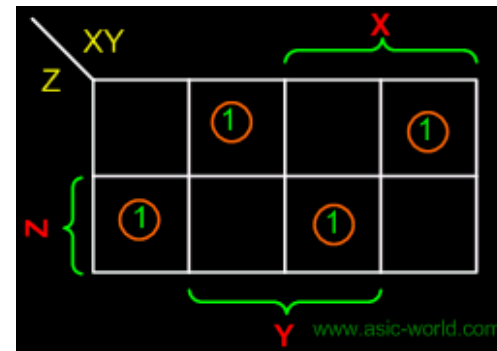

$$\text{SUM} = X \oplus Y \oplus Z$$

 


$$C = XY + YZ + XZ$$


Full Adder



$$\text{SUM} = X \oplus Y \oplus Z$$

 

$$\text{CARRY} = XY + YZ + XZ$$

 

Symbol:



n-bit (Carry Ripple) Adder



- An **n-bit adder** used to add two n-bit binary numbers can be built by connecting **n full adders in series**. Each full adder represents a bit position **j** (from **0** to **n-1**).
- Each carry out **C-out** from a full adder at position **j** is connected to the carry in **C-in** of the full adder at higher position **j+1**.

The output of a full adder at position j is given by:

$$S_j = X_j \oplus Y_j \oplus C_j$$

$$C_{j+1} = X_j \cdot Y_j + X_j \cdot C_j + Y_j \cdot C_j$$

- In the expression of the sum C_j must be generated by the full adder at lower position j. The propagation delay in each full adder to produce the carry is equal to two gate delays = 2 D. Since the generation of the sum requires the propagation of the carry from the lowest position to the highest position, the total propagation delay of the adder is approximately:
 - **Total Propagation delay = 2 nD**


4-bit Carry Ripple Adder




- Adds two 4-bit numbers:

$$X = X_3 X_2 X_1 X_0$$

$$Y = Y_3 Y_2 Y_1 Y_0$$

 


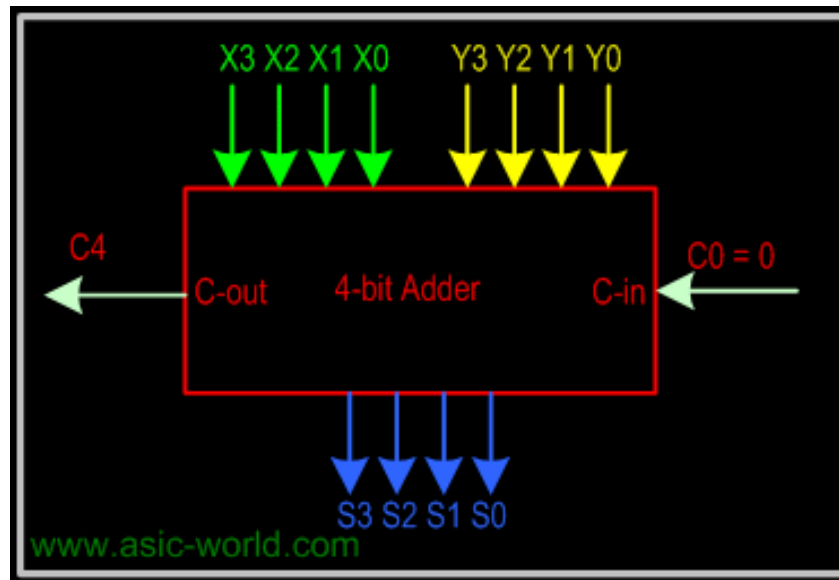- Producing the sum: $S = S_3 S_2 S_1 S_0$,
 $C_{out} = C_4$ from the most significant position $j=3$
 - Total Propagation delay = $2 nD = 8D$ or 8 gate delays!





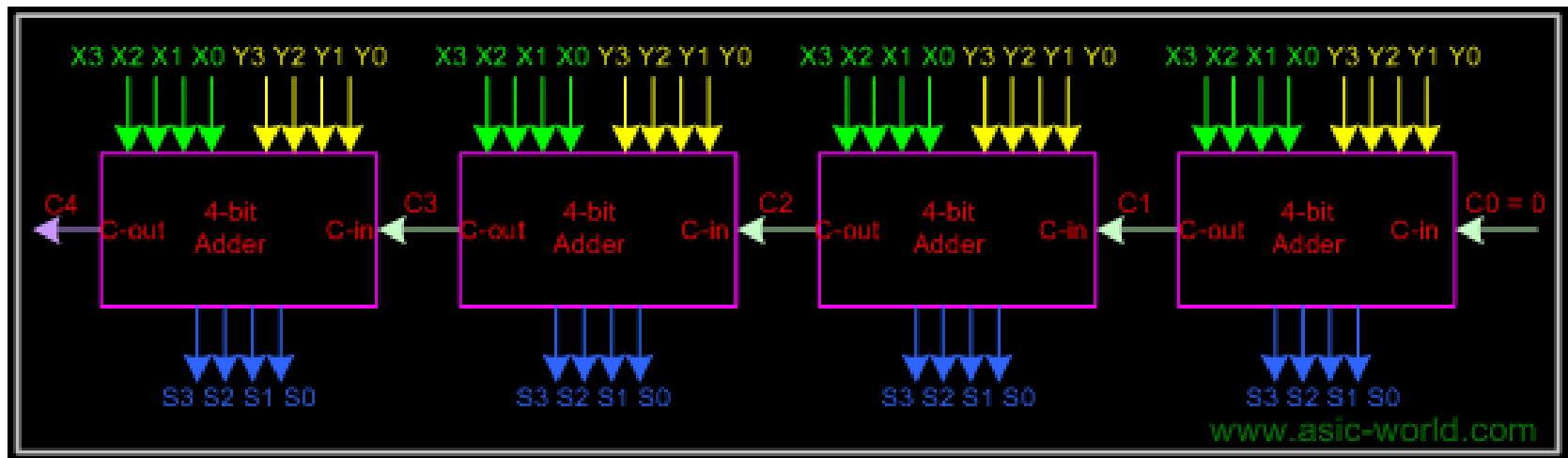- Example: 16-bit adder using 4x4-bit adders.
 - Adds two 16-bit inputs **X** (bits X_0 to X_{15}), **Y** (bits Y_0 to Y_{15}) producing a 16-bit Sum **S** (bits S_0 to S_{15}) and a carry out **C₁₆** from the most significant position



- Propagation delay for 16-bit adder = 4 x propagation delay of 4-bit adder = 4 x 2 nD = 4 x 8D = 32 D or 32 gate delays

Carry Look-Ahead Adder



- The delay generated by an N-bit adder is proportional to the length N of the two numbers X and Y that are added because the carry signals have to propagate from one full-adder to the next.
- For large values of N, the delay becomes unacceptably large so that a special solution needs to be adopted to accelerate the calculation of the carry bits.
- This solution involves a "look-ahead carry generator" which is a block that simultaneously calculates all the carry bits involved.
- The design of the look-ahead carry generator involves two Boolean functions named Generate and Propagate. For each input bits pair these functions are defined as:

$$G_i = X_i \cdot Y_i$$

$$P_i = X_i + Y_i$$

Carry Look-Ahead Adder





- For a four-bit adder the carry-outs are calculated as follows:

$$\text{carry_out}_0 = G_0 + P_0 * \text{carry_in}_0$$

$$\text{carry_out}_1 = G_1 + P_1 * \text{carry_out}_0 = G_1 + P_1G_0 + P_1P_0 * \text{carry_in}_0$$

$$\text{carry_out}_2 = G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0 * \text{carry_in}_0$$
  
$$\text{carry_out}_3 = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0 + P_3P_2P_1 * \text{carry_in}_0$$





- Subtractor circuits take two binary numbers as input and subtract one binary number input from the other binary number input.
- Similar to adders, it gives out two outputs, difference and borrow.
- There are two types of subtractors:
 - Half Subtractor.
 - Full Subtractor.

Half Subtractor




- The half-subtractor is a combinational circuit which is used to perform subtraction of two bits.
- It has two inputs, X (minuend) and Y (subtrahend) and two outputs D (difference) and B (borrow).

- Truth Table:

X	Y	D	B
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Boolean expressions:

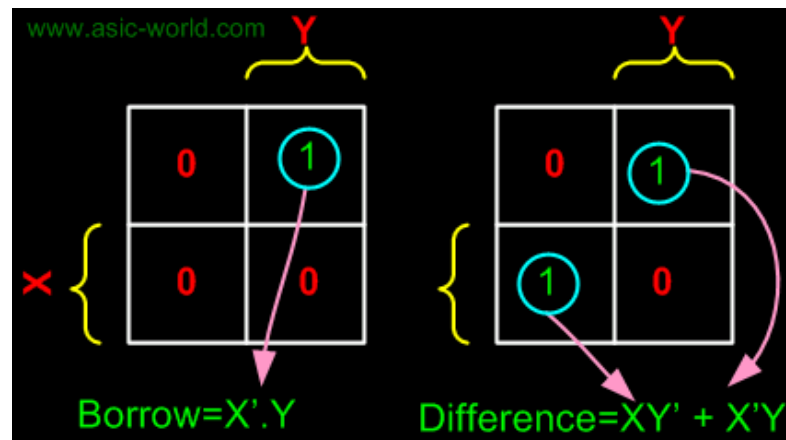

$$\text{Difference} = XY' + X'Y$$

$$\text{Borrow} = X' Y$$


Half Subtractor




$$\text{Difference} = XY' + X'Y$$

$$\text{Borrow} = X' Y$$

Circuit:

 

Symbol:

 

Full Subtractor



- A full subtractor is a combinational circuit that performs subtraction involving three bits, namely minuend, subtrahend, and borrow-in.
- Truth Table:

X	Y	B _{in}	D	B _{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$D = X \oplus Y \oplus B_{in}$$

$$B = X'Y + X'B_{in} + YB_{in}$$


Full Subtractor




$$D = X \oplus Y \oplus \text{Bin}$$

$$B = X'Y + X'B_{\text{in}} + YB_{\text{in}}$$

- Circuit:

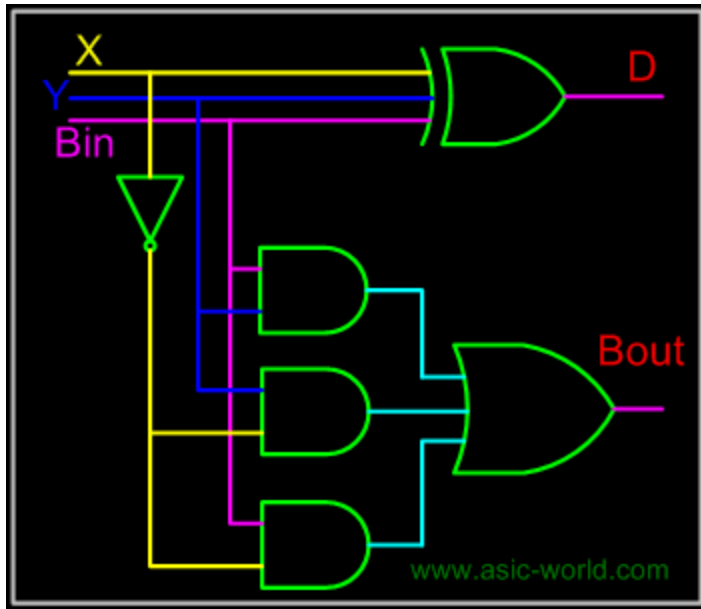


Symbol:

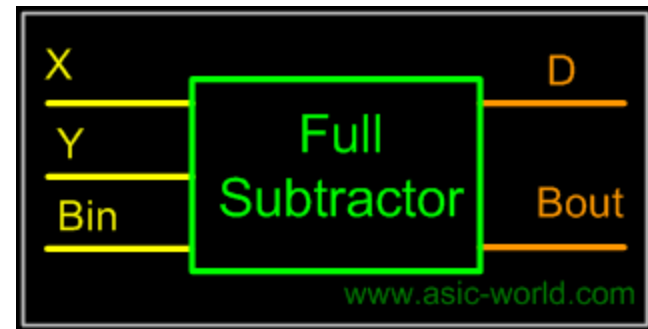

Full Subtractor



 
- Full subtractor composed by 2 half subtractors:



Parallel Binary Subtractor



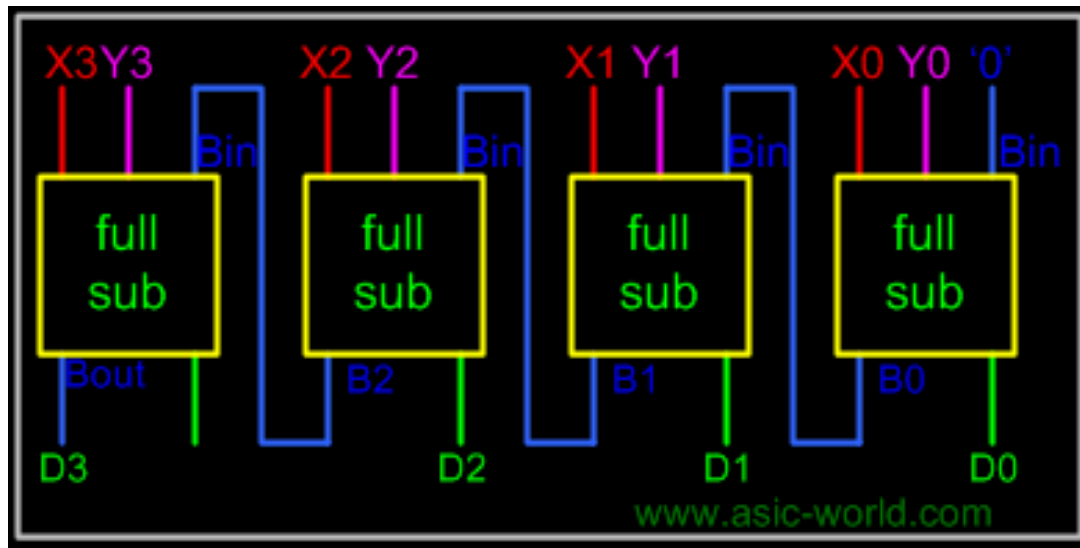
- Parallel binary subtractor can be implemented by cascading several full-subtractors.
- Block level representation of a 4-bit parallel binary subtractor, which subtracts 4-bit $Y_3Y_2Y_1Y_0$ from 4-bit $X_3X_2X_1X_0$. It has 4-bit difference output $D_3D_2D_1D_0$ with borrow output B_{out}



Serial Binary Subtractor



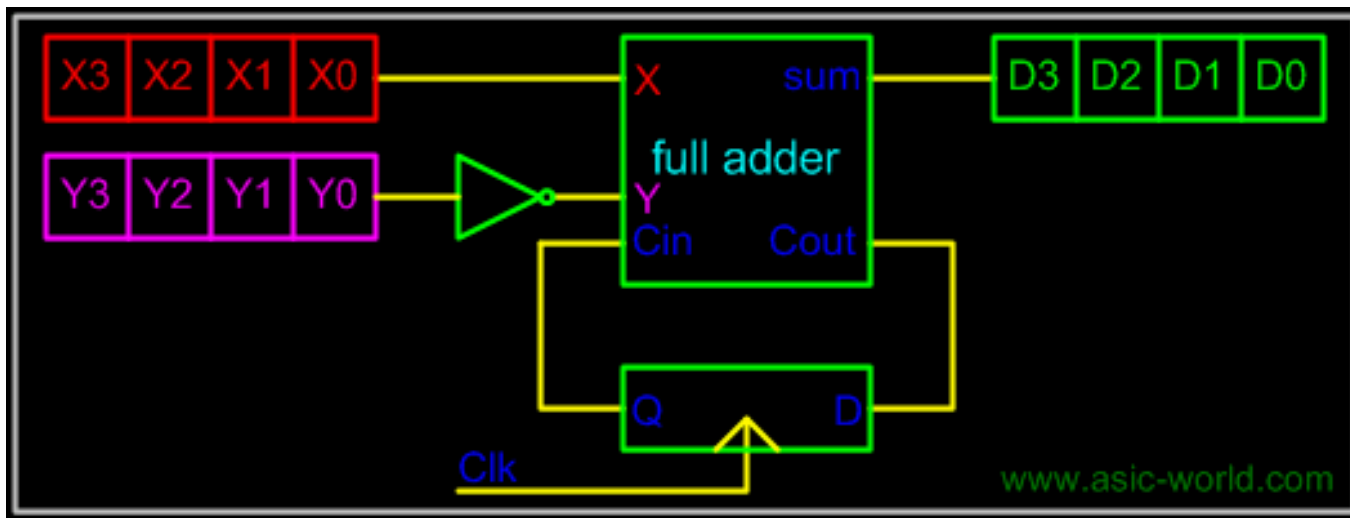- A serial subtractor can be obtained by converting the serial adder using the 2's complement system.
- The subtrahend is stored in the Y register and must be 2's complemented before it is added to the minuend stored in the X register.
- The circuit for a 4-bit serial subtractor using full-adder:




Multipliers



- Multiplication is achieved by adding a list of shifted multiplicands according to the digits of the multiplier.
- An n -bit \times n -bit multiplier can be realized in combinational circuitry by using an array of $n-1$ n -bit adders where each adder is shifted by one position.
- For each adder one input is the shifted multiplicand multiplied by 0 or 1 (using AND gates) depending on the multiplier bit, the other input is n partial product bits.
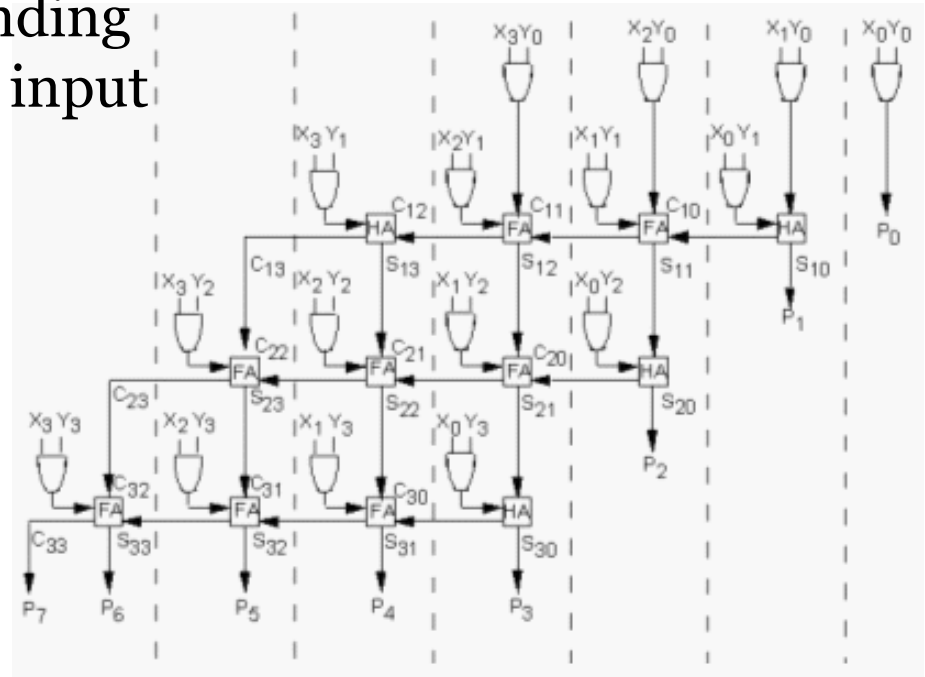
$$\begin{array}{r} 10011 \times 1001 \\ \hline 10011 \\ 00000 \\ 00000 \\ 10011 \\ \hline 10101011 \end{array}$$






- The binary divisions are performed in a very similar manner to the decimal divisions.
- Thus, the second number is repeatedly subtracted from the figures of the first number after being multiplied either with '1' or with '0'.
- The multiplication bit ('1' or '0') is selected for each subtraction step in such a manner that the subtraction result is not negative.
- The division result is composed from all the successive multiplication bits while the remainder is the result of the last subtraction step.

$$\begin{array}{r} 1101011 : 101 = 10101 \\ \underline{101} \times 1 \leftarrow \\ 11 - \\ \underline{101} \times 0 \leftarrow \\ 110 - \\ \underline{101} \times 1 \leftarrow \\ 11 - \\ \underline{101} \times 0 \leftarrow \\ 111 - \\ \underline{101} \times 1 \leftarrow \\ 10 \end{array}$$




■ Adder/Subtractor

S	Function	Comment
0	$X + Y$	Addition
1	$X + Y' + 1$	Subtraction

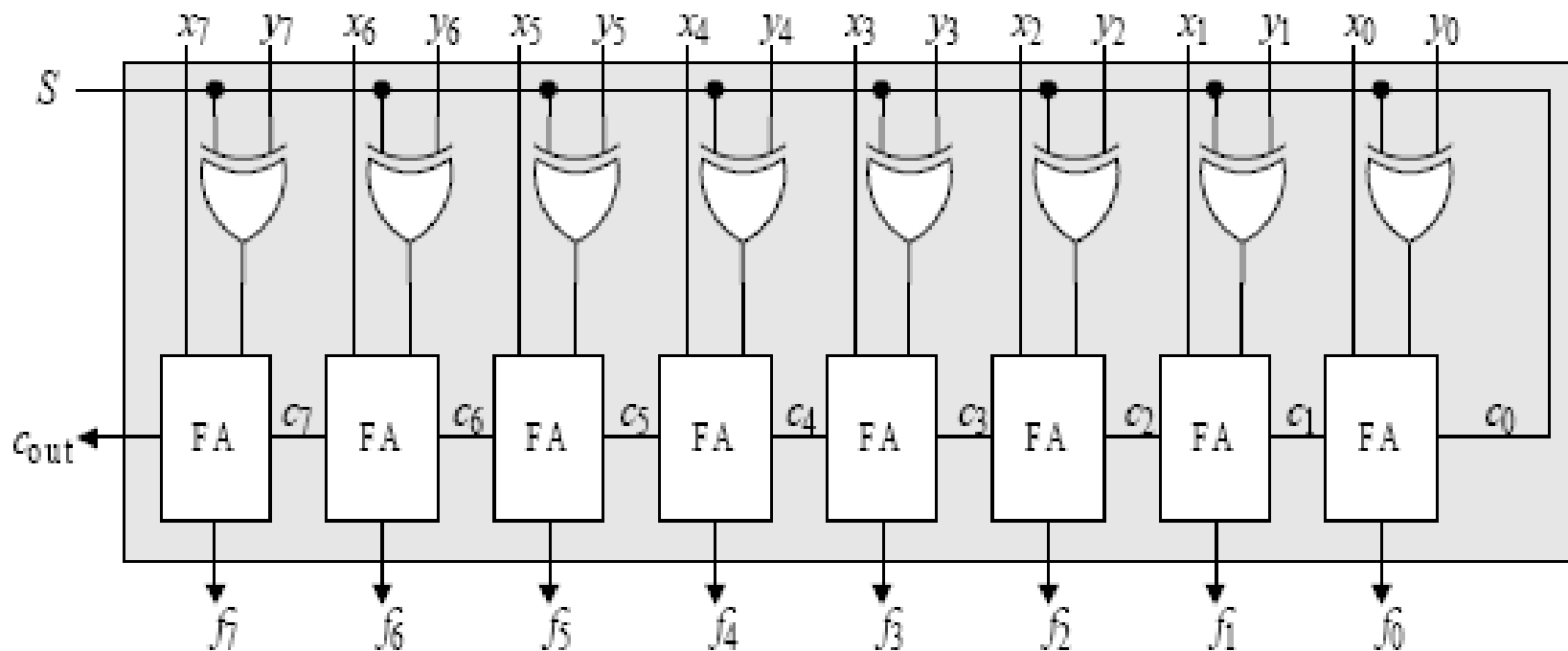



Arithmetic-Logic Unit (ALU)

 

Arithmetic Extender (AE)

Logic Extender (LE)

M	S ₁	S ₀	Function Name
1	0	0	Decrement
1	0	1	Add
1	1	0	Subtract
1	1	1	Increment

M	S ₁	S ₀	Function Name
0	0	0	Complement
0	0	1	AND
0	1	0	Identity
0	1	1	OR



- Questions?!

